

 


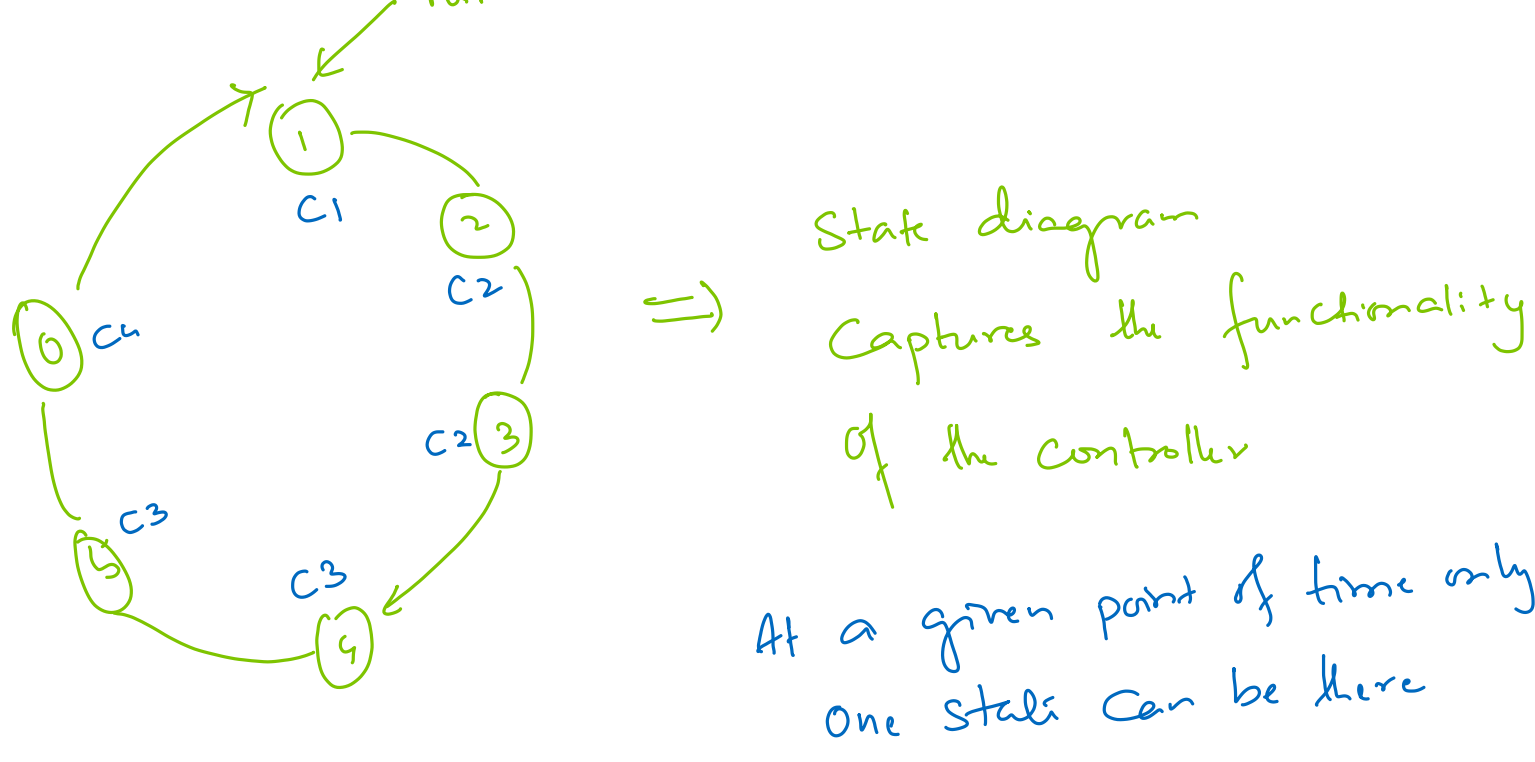1. FINITE STATE MACHINES

Condition \rightarrow binary value \rightarrow FFS (output)
Persists for a certain amount of time



 A Valid State should persist for atleast 1 clock cycle.




Coding the State machine:

- \rightarrow Come up with a state diagram
- \rightarrow Identify the number of States

Find the minimum number of ffs needed to generate the 'n' states
 $2^n \geq N$
 $n < 3 \times$
 $n > 3 \times$
 $2^n \geq 6$
 $n = 3$ optimal

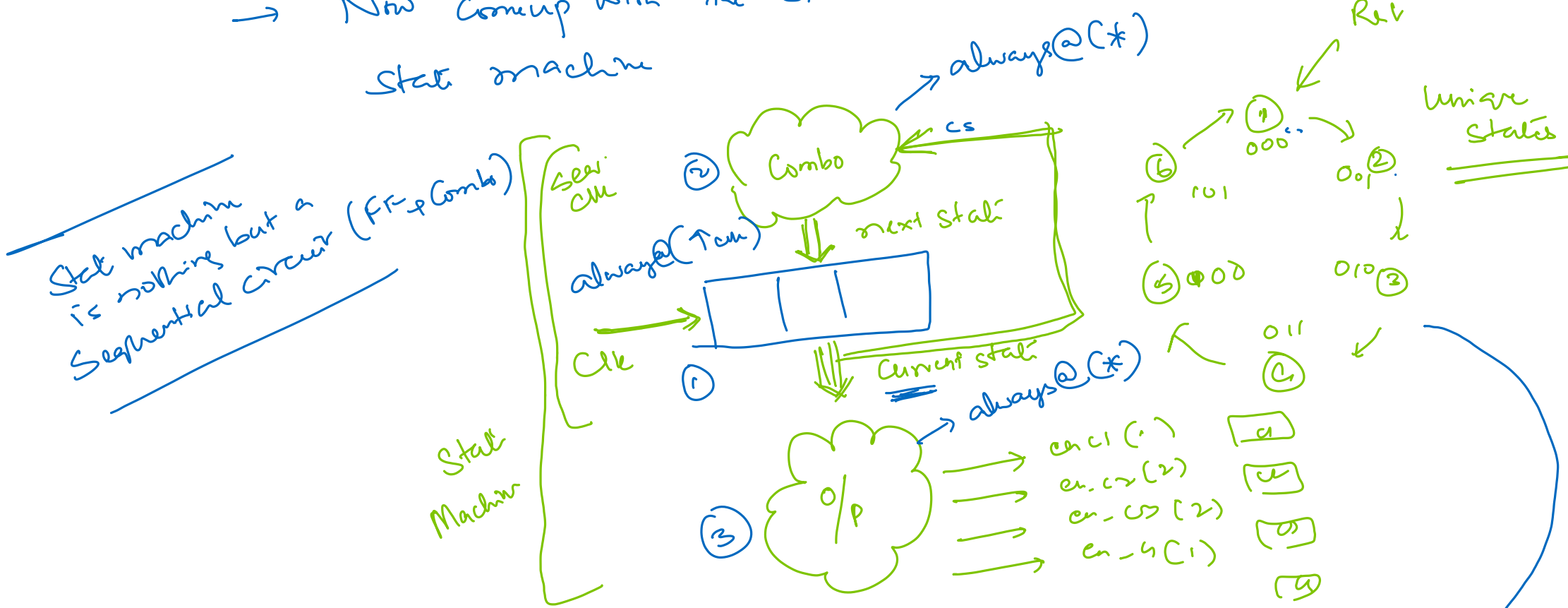Now coming with the standard template for a state machine




FSM is generally coded with 3 always blocks


```
reg [2:0] cs;
always@ (*)
if (reset)
    cs <= initial_state;
else
    cs <= next_state;

always@ (*)
begin
    case (cs)
        3'b000: Next_state = 3'b001;
        3'b001: Next_state = 3'b010;
        3'b010: Next_state = 3'b011;
        3'b011: Next_state = 3'b100;
        3'b100: Next_state = 3'b101;
        3'b101: Next_state = 3'b110;
        3'b110: Next_state = 3'b111;
        3'b111: Next_state = 3'b000;
    endcase
end
```


How does the top level module look like?

 

2. Another Scenario

 

3. Sequence detector

 

No. of States = 4
No. of FFS = 2

2 pass state machine

